
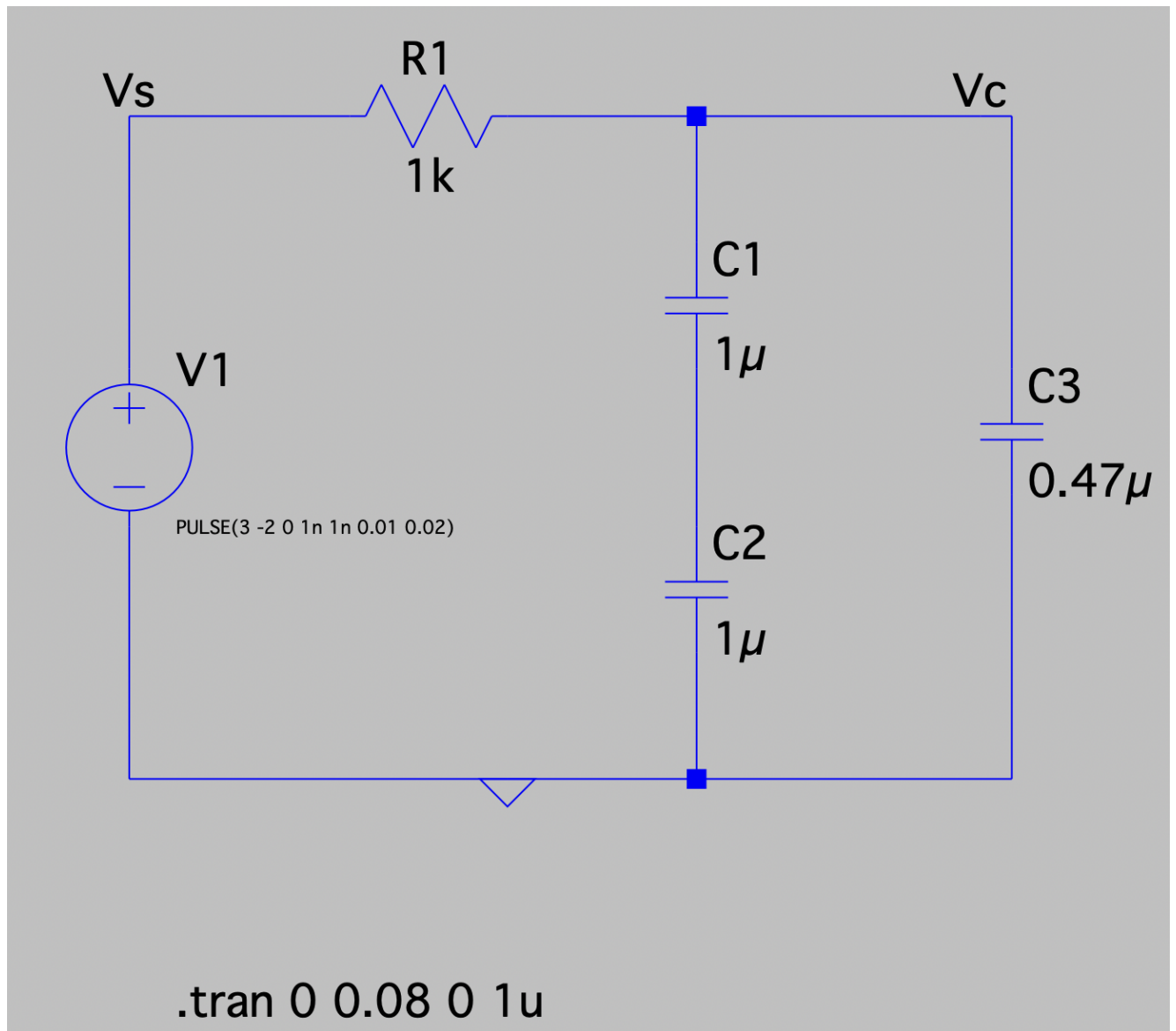


EXPERIMENT 8:

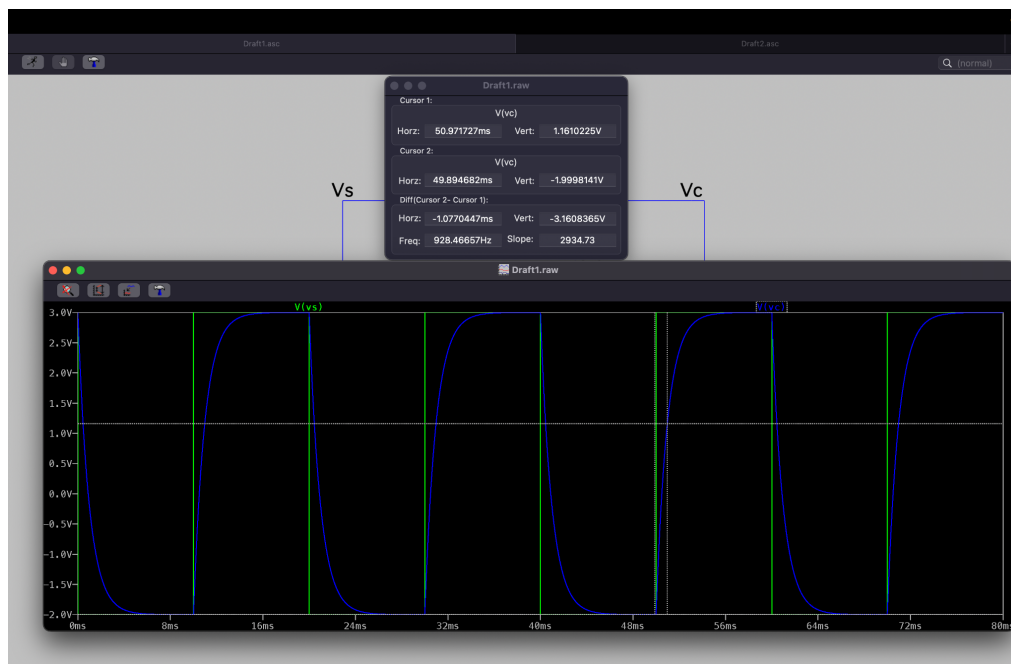

Graph:




From the circuit, Time constant, τ = (time_diff) = 1.07 ms


From theory, τ = $RC(eq)$ = 1 ms

Observation: The simulated time constant and theoretical time constant are close to each other.


EXPERIMENT 9:

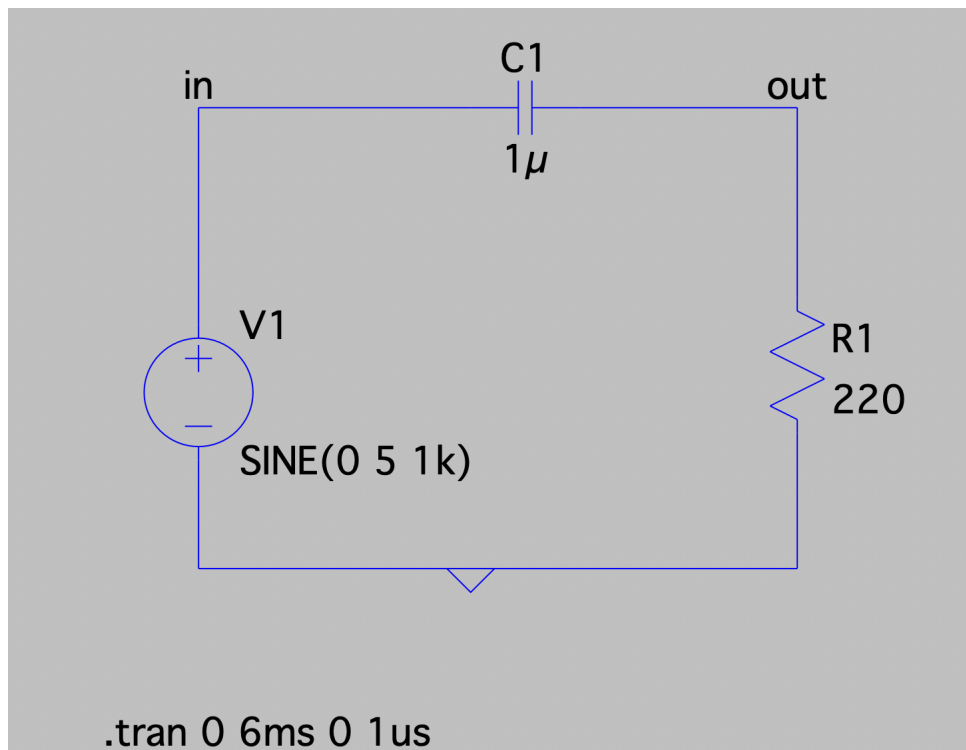


GRAPH:
(For 1kHz frequency):

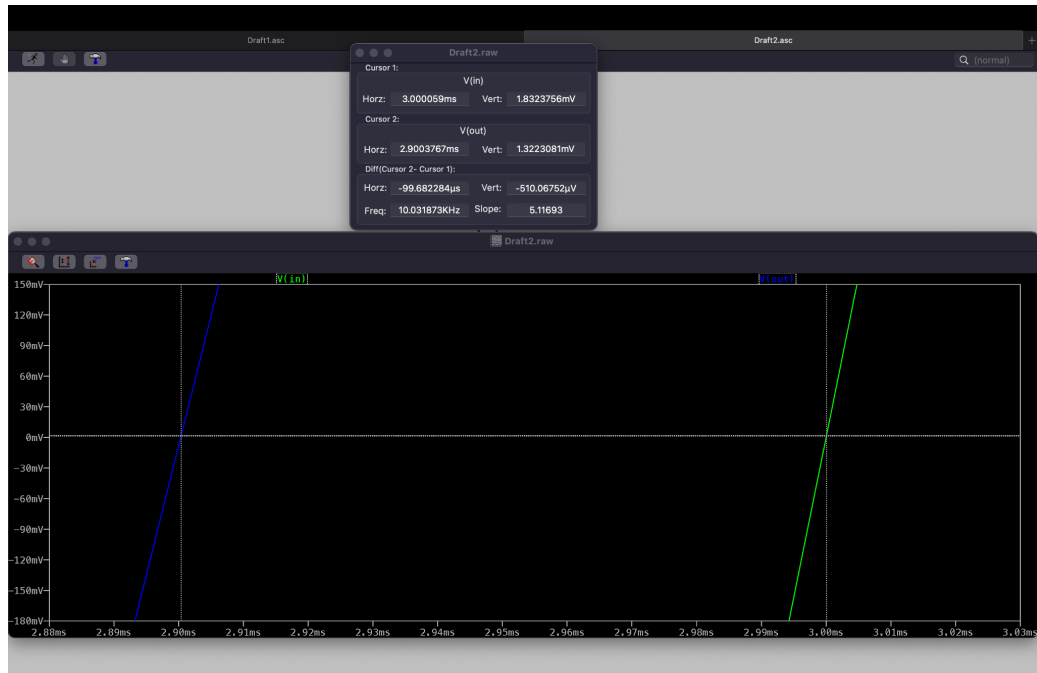

(For 2kHz frequency):

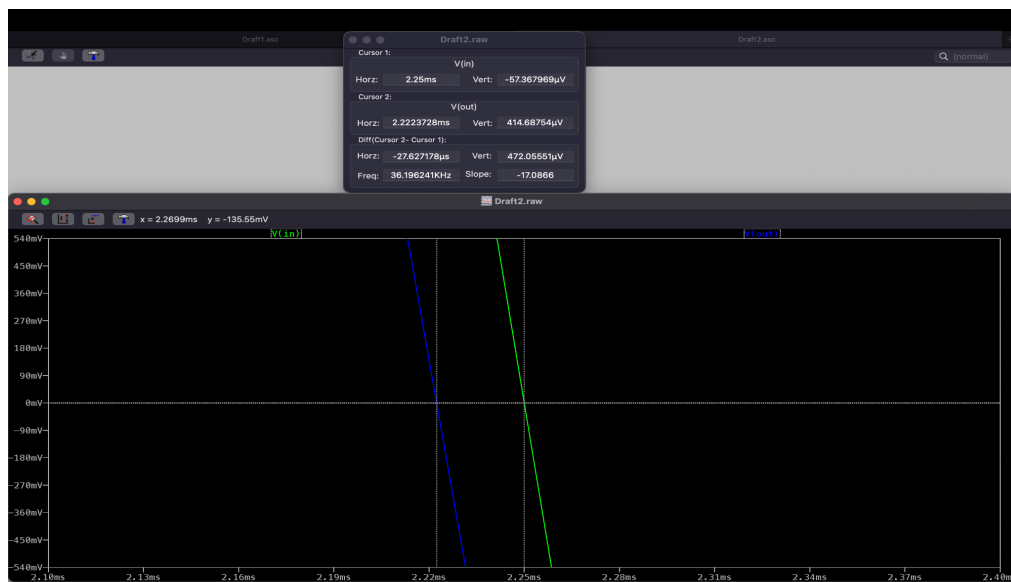

(FOR 500 Hz frequency):

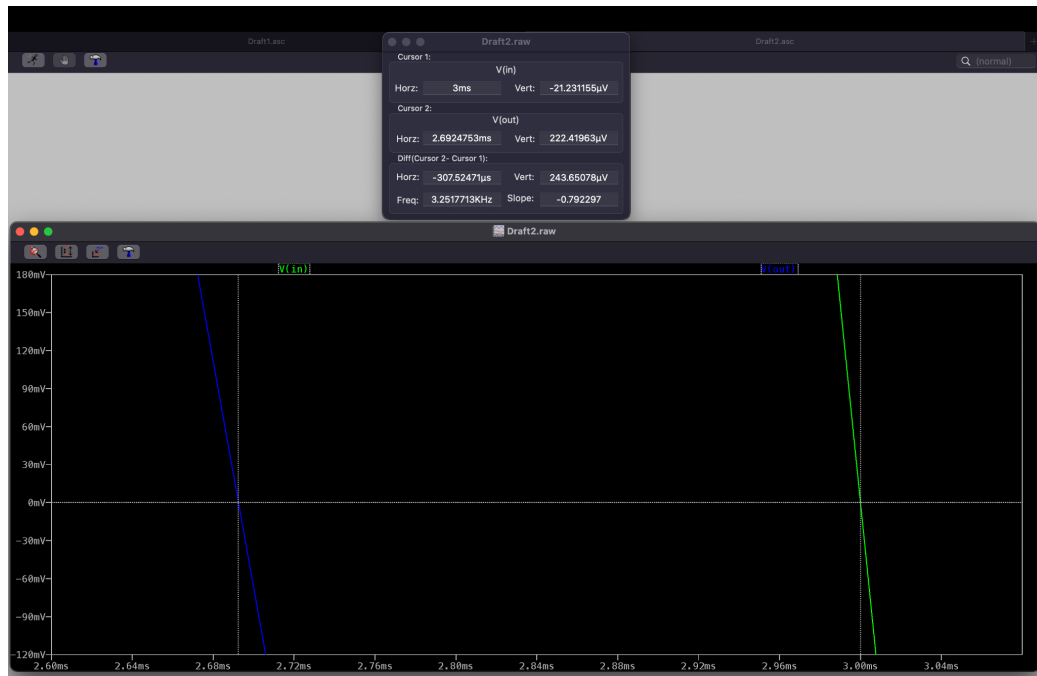

Phase Difference Calculation:

- **For 1 kHz:**
Phase difference = $99.68 \times (10^{-6}) \times 1000 \times 360$
Phase difference = 35.89°
- **For 2 kHz:**
Phase difference = $27.62 \times (10^{-6}) \times 2000 \times 360$
Phase difference = 19.89°
- **For 500 Hz:**
Phase difference = $307.52 \times (10^{-6}) \times 500 \times 360$
Phase difference = 55.36°

